

## CS M51A/EE M16 FINAL EXAM

– closed books and notes –

(8 problems, 180 minutes)

**PLEASE BE SYSTEMATIC, ORGANIZED, and NEAT:**

– this will be considered in the grading.


December 13, 2002

Name: SOLUTIONS

| Problem | Points | Score |
|---------|--------|-------|
| 1       | 20     |       |
| 2       | 10     |       |
| 3       | 14     |       |
| 4       | 12     |       |
| 5       | 8      |       |
| 6       | 13     |       |
| 7       | 13     |       |
| 8       | 10     |       |
| Total   | 100    |       |

**Problem 1.** (20 points) Design a sequential system which recognizes the pattern 0101011.

 a) [6 points] Complete the following state diagram. Each state is labeled with a sequence that it "recognizes".



The correspondence between the state assignment and sequence that it detects is shown in the next table.


| State | Sequence |
|-------|----------|
| $S_0$ | start    |
| $S_1$ | 0        |
| $S_2$ | 01       |
| $S_3$ | 010      |
| $S_4$ | 0101     |
| $S_5$ | 01010    |
| $S_6$ | 010101   |

b) [4 points] Encode these states using three state variables ( $y_2, y_1, y_0$ ) so that the state assignment of state  $S_i$  is the radix-2 representation of  $i$ . Complete the state and transition table:

| PS    | $y_2 y_1 y_0$ | Input   |         | Input   |         |
|-------|---------------|---------|---------|---------|---------|
|       |               | $x = 0$ | $x = 1$ | $x = 0$ | $x = 1$ |
| $S_0$ | 000           | 000,0   | 000,0   | 000     | 000     |
| $S_1$ | 001           | 001,0   | 010,0   | 000     | 011     |
| $S_2$ | 010           | 011,0   | 000,0   | 001     | 010     |
| $S_3$ | 011           | 001,0   | 100,0   | 010     | 111     |
| $S_4$ | 100           | 101,0   | 000,0   | 001     | 100     |
| $S_5$ | 101           | 001,0   | 110,0   | 100     | 011     |
| $S_6$ | 110           | 101,0   | 000,1   | 011     | 110     |

|       |       |       |       |
|-------|-------|-------|-------|
| $S_0$ | $S_1$ | $S_3$ | $S_2$ |
| $S_4$ | $S_5$ | $S_7$ | $S_6$ |
| $S_0$ | $S_1$ | $S_3$ | $S_2$ |

 c) [6 points] Implement the network using NAND gates and T flip-flops. Indicate the T inputs in the state table. Give minimal sum of products expressions for T inputs. Show the logic diagram of the network.




$$T_2 = x y_2 y_0' + x y_1 y_0 + x' y_2 y_0$$

$$T_1 = y_1 y_0 + y_2 y_1 + x y_0 + x y_1$$

$$T_0 = x' y_0' + x y_0$$

$$z = x y_1 y_2$$

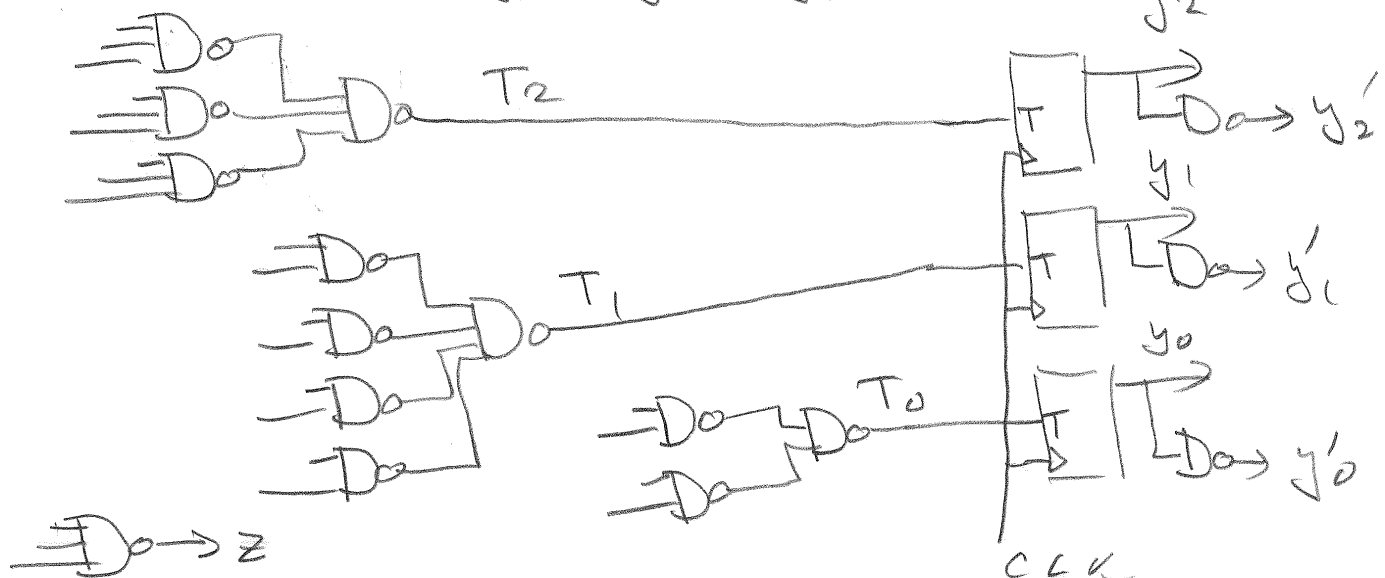

d) [4 points] If the propagation delays are  $t_p = 3.5ns$ ,  $t_{su} = 0.9ns$ ,  $t_{NAND} = 2ns$ ,  $t_{in} = 1.5ns$ , and  $t_{out} = 2.5ns$ , determine the maximum clock frequency.

$$T_{min} = \max \left[ (t_{in} + t_{su}^x(\text{net})), \right. \\ (t_p(\text{cell}) + t_{su}^y(\text{net})), \\ \left. (t_p(\text{net}) + t_{out}) \right]$$

$$t_{su}^x(\text{net}) = 2.2 + 0.9 = 4.9 \mu s$$

$$t_{su}^y(\text{net}) = 3.2 + 0.9 = 6.9 \mu s$$


$$t_p(\text{net}) = 3.5 + 2 = 5.5 \mu s$$

$$T_{min} = \max \left[ \overset{6.9}{(1.5 + 4.9)}, \overset{10.4}{(3.5 + 6.9)}, \right. \\ \left. \underset{8}{(5.5 + 2.5)} \right]$$

$$= 10.4 \mu s$$

$$f_{max} = \frac{1}{10.4 \times 10^{-9}} \approx 100 \text{ MHz}$$

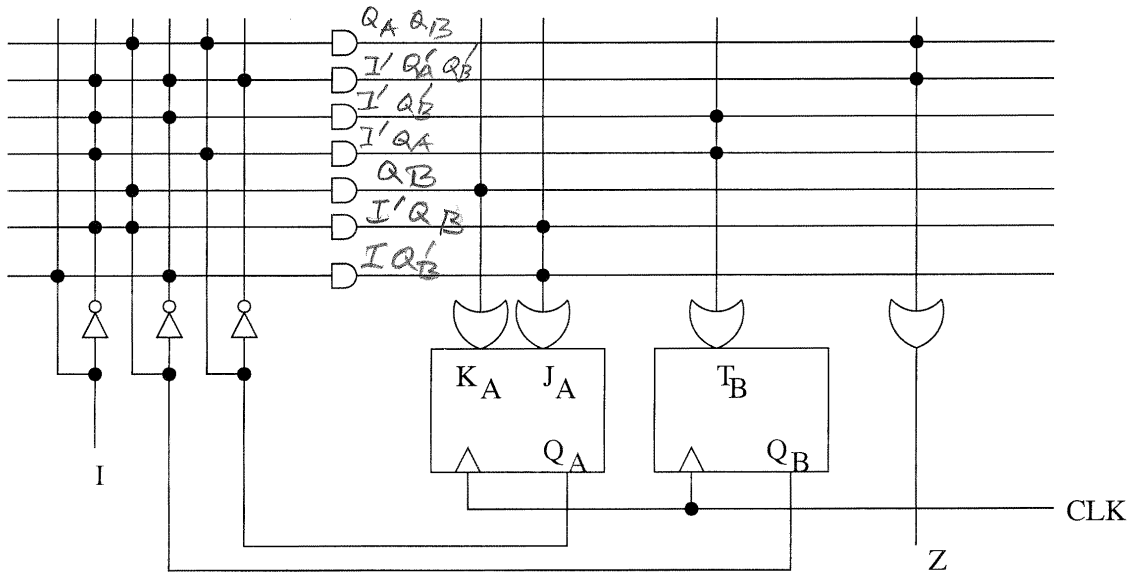**Problem 2.** (10 points) Derive the state transition/output table for the implementation of the sequential system shown in the figure below. The next state and output functions are implemented by a PLA structure. The machine has one input  $I$  and one output  $Z$ . Show expressions for the flip-flop inputs. Show the state transition/output table.



$$J_A = I'Q_B + IQ_B' = I \oplus Q_B$$

$$K_A = Q_B$$

$$T_B = I'(Q_A + Q_B')$$

$$Z = I'Q_A'Q_B' + Q_AQ_B$$

| PS( $Q_AQ_B$ ) | I | $J_A$ | $K_A$ | $T_B$ | NS | Z |
|----------------|---|-------|-------|-------|----|---|
| 00             | 0 | 0     | 0     | 1     | 01 | 1 |
| 00             | 1 | 1     | 0     | 0     | 10 | 0 |
| 01             | 0 | 1     | 1     | 0     | 11 | 0 |
| 01             | 1 | 0     | 1     | 0     | 01 | 0 |
| 10             | 0 | 0     | 0     | 1     | 11 | 0 |
| 10             | 1 | 1     | 0     | 0     | 10 | 0 |
| 11             | 0 | 1     | 1     | 1     | 00 | 1 |
| 11             | 1 | 0     | 1     | 0     | 01 | 1 |

**Problem 3.** (14 points)

(a) [8 points] Design a cyclic counter with the output sequence 0, 1, 4, 7, 6, 3, 0, 1, ... (of period 6) using JK flip-flops and AND, OR, NOT gates as needed. Assume that the input  $x$  is always 1. Select a state assignment that is the same as the coding for the output, that is  $z(t) = s(t)$ . Show the state/output table. Minimize all expressions. Show the logic diagram of the counter.

State/output table:

| PS    | NS    | PS<br>$Q_2 Q_1 Q_0$ | NS<br>$Q_2 Q_1 Q_0$ | JK    |
|-------|-------|---------------------|---------------------|-------|
| $S_0$ | $S_1$ | 0 0 0               | 0 0 1               | 0 0 1 |
| $S_1$ | $S_4$ | 0 0 1               | 1 0 0               | 1 0 0 |
| $S_4$ | $S_7$ | 1 0 0               | 1 1 1               | 1 1 1 |
| $S_7$ | $S_6$ | 1 1 1               | 1 1 0               | 1 1 0 |
| $S_6$ | $S_3$ | 1 1 0               | 0 1 1               | 0 1 1 |
| $S_3$ | $S_0$ | 0 1 1               | 0 0 0               | 0 0 0 |

JK  
NS  
PS

| PS | NS    |
|----|-------|
| 0  | 0- 1- |
| 1  | -1 -0 |

JK  
 $S_2, S_5 - d.c.$

$J_2$

| Q0      |
|---------|
| 0 1 0 - |
| Q2      |
| - - - - |

Q1

$J_1$

| Q0      |
|---------|
| 0 0 - - |
| Q2      |
| 1 - - - |

Q1

$J_0$

| Q0      |
|---------|
| 1 - - - |
| Q2      |
| 1 - - 1 |

Q1

$K_2$

| Q0      |
|---------|
| - - - 1 |
| Q2      |
| 0 - 0 1 |

Q1

$K_1$

| Q0      |
|---------|
| - - 1 - |
| Q2      |
| - - 0 0 |


Q1

$K_0$



| Q0      |
|---------|
| - 1 1 - |
| Q2      |
| - - 1 - |

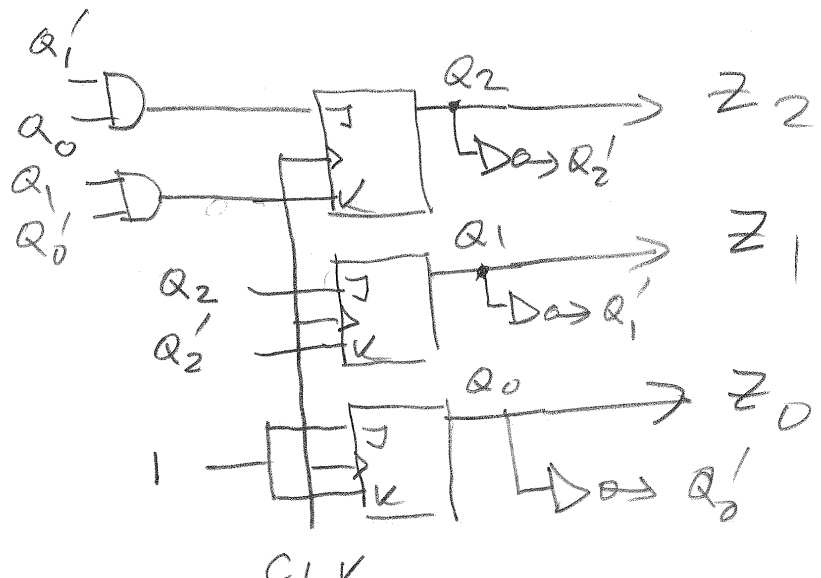Q1



$J_0 = 1$   
 $K_0 = 1$   
 $J_1 = Q_2$   
 $K_1 = Q_2'$   
 $J_2 = Q_1' Q_0$   
 $K_2 = Q_1 Q_0'$



  (b) [6 points] Design the cyclic counter defined in part (a) using the "one flip-flop per state" approach with D flip-flops. To obtain the output, use a suitable standard combinational module - do not design a gate network! Show all connections. Show the initial state of this implementation.



 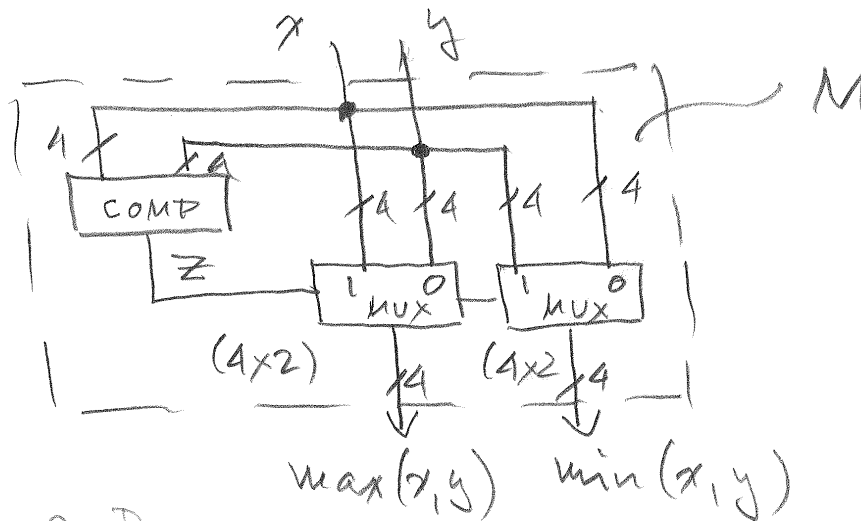**Problem 4.** (12 points) Design a hierarchical combinational network that finds the second largest of four nonnegative integers  $A, B, C, D$ . Each integer is represented by four bits. You may use only the following module types:  $4 \times 2$ -input multiplexer and four-bit comparator. The single-bit output of the comparator is  $z$ . If the first integer is larger than the second, the output is  $z = 1$ . Otherwise,  $z = 0$ . Define first your basic module and then design the network using your module. Indicate all inputs and connections on the modules being used.



\* can be simplified (eliminate one  $4 \times 2$  MUX)




**Problem 5.** (8 points) Implement the following systems using standard combinational modules (no gate networks allowed):

Input:  $x \in \{0, 1, 2, 3, 4, 5, 6, 7\}$ , represented in binary by  $\underline{x} = \{x_2, x_1, x_0\}$ ,  $x_i \in \{0, 1\}$ .

Output:  $y \in \{0, 1, 2, 3, 4, 5, 6, 7\}$ , represented in binary by  $\underline{y} = \{y_2, y_1, y_0\}$ ,  $y_i \in \{0, 1\}$

Function:  $y = (3x + 2) \bmod 8$

|     |   |   |   |   |   |   |   |   |
|-----|---|---|---|---|---|---|---|---|
| $x$ | 0 | 1 | 2 | 3 | 4 | 5 | 6 | 7 |
| $y$ | 2 | 5 | 0 | 3 | 6 | 1 | 4 | 7 |

 

**Problem 6.** (13 points)

a) [8 points] Complete the following table. If an entry in the table cannot be filled properly, explain why and how to fix it. Representation values are given in the decimal number system.

| Number system | Number of digits $n$ | Signed integer $x$ | Representation value $x_R$ | Digit-vector $X$ |
|---------------|----------------------|--------------------|----------------------------|------------------|
| 2's compl.    | 7                    | -35                | 93                         | 1011101          |
| 1s' compl.    | 8                    | -86                | 169                        | 10101001         |
| 2's compl.    | 9                    | -218               | 294                        | 100100110        |
| 2's compl.    | 6                    | -33                | -                          | -                |

↑ requires  $n=7$

b) [5 points] Compute  $z = a + 2b - c$  in 2's complement for  $a = -9$ ,  $b = 17$ , and  $c = -77$ . Perform calculations on bit-vectors representing  $a$ ,  $b$  and  $c$  and show every step of your work. How many bits should  $z$  have to represent the correct result? Check your work by showing, for each step, the corresponding values in decimal number system.

$$z = -9 + 34 + 77 = 102$$


in 2's complement  $\Rightarrow$  8 bits

$$\begin{array}{r}
 a = -9 \\
 2b = 34 \\
 -c = 77 \\
 \hline
 102
 \end{array}$$

$$\begin{array}{r}
 11110111 \\
 00100010 \\
 01001101 \\
 \hline
 01100110
 \end{array}$$

**Problem 7.** (13 points) Design a sequential system specified by the following state transition and output table using a modulo-8 counter with parallel load as the state register, a 8-to-1 multiplexer for the CNT input and NAND gates. Assume  $LD = CNT'$ . The design must take advantage of the count and parallel mode capabilities of the counter. Show a state diagram and all your work.

|       | PS<br>$Q_2Q_1Q_0$ | Input<br>$x = 0$ | Input<br>$x = 1$ |
|-------|-------------------|------------------|------------------|
| $S_0$ | 000               | 000,0            | 001,0            |
| $S_1$ | 001               | 000,0            | 010,0            |
| $S_2$ | 010               | 000,0            | 011,0            |
| $S_3$ | 011               | 100,0            | 011,0            |
| $S_4$ | 100               | 101,0            | 001,0            |
| $S_5$ | 101               | 000,1            | 001,0            |
|       |                   | $NS, z$          | $NS, z$          |

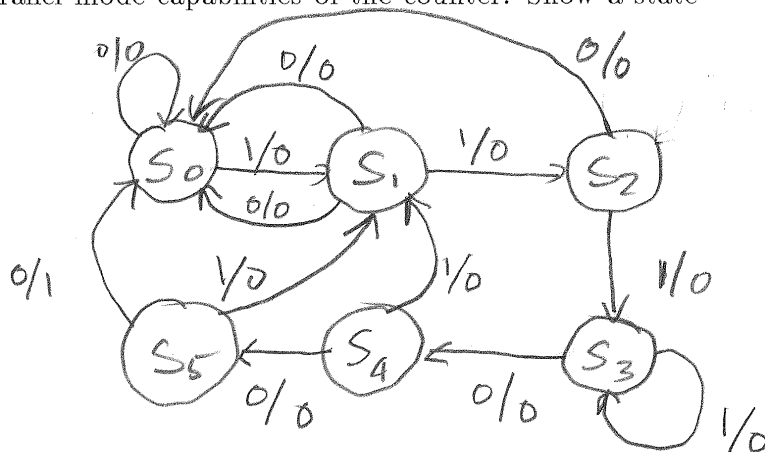

$$CNT = S_0x + S_1x + S_2x + S_3x' + S_4x'$$

$$LD = CNT'$$

$$I_2 I_1 I_0$$

$$0 \ 0 \ 0 \quad \text{if } S_0 + S_1 + S_2 + S_5x'$$

$$0 \ 0 \ 1 \quad \text{if } S_4 + S_5x$$

$$0 \ 1 \ 1 \quad \text{if } S_3$$

$$I_2 = 0 \quad I_1 = Q_0Q_1 \quad I_0 = Q_0Q_1 + Q_2x + Q_2Q_0'$$

$$I_1$$


|       | $Q_0$   |
|-------|---------|
| $Q_2$ | 0 0 1 0 |
| $Q_1$ | 0 0 - - |

$$I_0$$

|       | $Q_0$ |   | $Q_1$ |
|-------|-------|---|-------|
|       | 0     | 0 | 1     |
| $Q_2$ | 0     | 1 | -     |

$$z = x Q_2 Q_0$$
 
$$Q_2 \equiv D_0 \rightarrow D_1 \rightarrow D_2 \rightarrow D_3 \rightarrow D_4 \rightarrow D_5 \rightarrow D_6 \rightarrow D_7$$



**Problem 8.** (10 points) Design a sequential system using combinational and sequential standard modules that detects when  $x(t-7, t-4) < x(t-3, t)$ , where four-bit input sequences are interpreted as positive integers.

